

Introduction

This is a collection of hints I refer to when I want to remember how I have done some task in NGSPICE in the past, but don't remember which simulation it was in. I hope that you, the reader, find some of this helpful. **This document is FREE to redistribute not for profit.**

Orcad Netlist

To ignore a component in the net listing, add a property NETLIST_IGNORE and set it to TRUE.

Pulse

Name	Parameter	Default Value	Units
V1	Initial value	-	V, A
V2	Pulsed value	-	V, A
TD	Delay time	0.0	sec
TR	Rise time	TSTEP	sec
TF	Fall time	TSTEP	sec
PW	Pulse width	TSTOP	sec
PER	Period	TSTOP	sec
PHASE	Phase	0.0	degrees

Example:


```
V1 1 0 PULSE (1 0.5 0 1u 1u 1m 2m)
```

A single pulse, without phase offset, is described by the following table:

Time	Value
0	V1
TD	V1
TD+TR	V2
TD+TR+PW	V2
TD+TR+PW+TF	V1
TSTOP	V1

and a practical example of it is here:

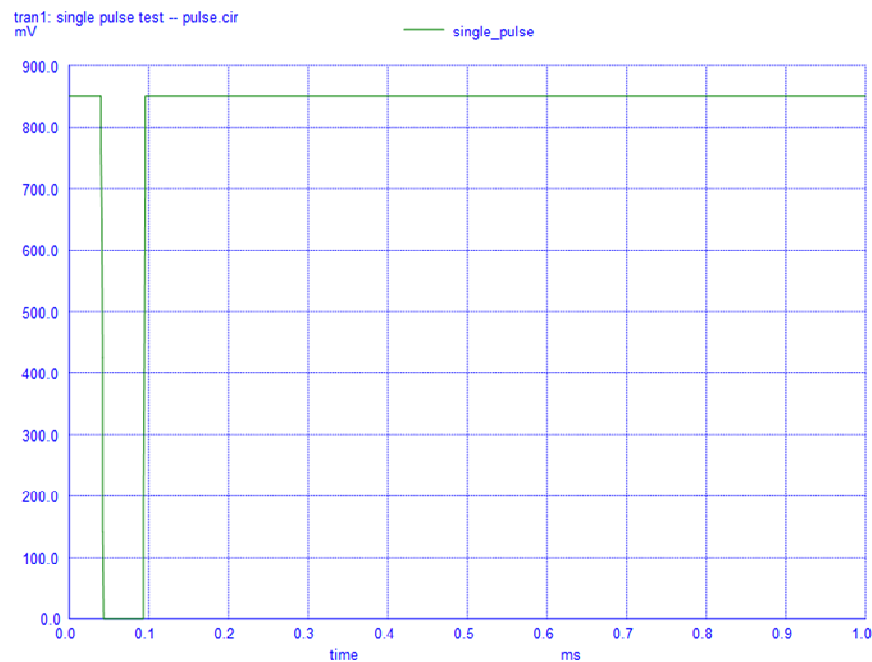v1 single_pulse 0 pulse (0.85 0 40u 3u 3u 50u 100m)




The .control options to make this plot are (svg format):

```
set hcopydevtype = svg
set svg_stropts = ( yellow Arial Arial )

set color0 = white
set color1 = blue
set color2 = green

hardcopy pulse.svg single_pulse
```


Switch

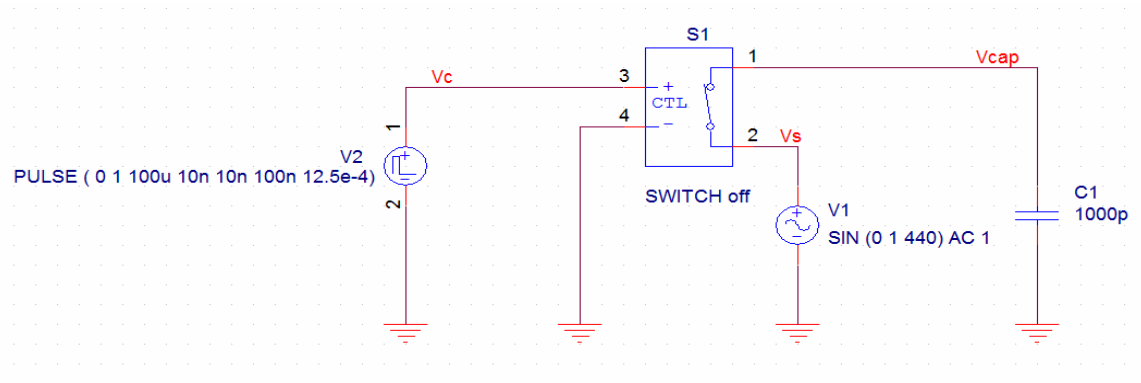

Netlist:

```
S1 VCAP VS VC 0 SWITCH off  
.model SWITCH SW Vt=0.5 Ron=0.001 Roff=1G
```

Coupled Inductor

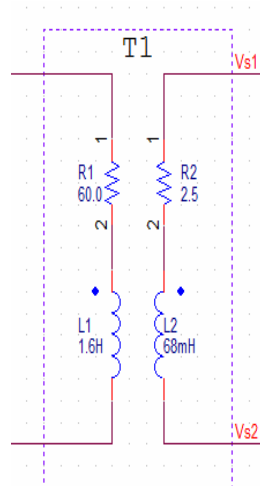

$$\frac{V_p}{V_s} = \sqrt{\frac{L_p}{L_s}}$$

.option RSHUNT=1Meg --- helps with the grounds

K12 L1 L2 0.99 --- coupling coefficient

XSPICE

Transfer function example of high pass filter parameterized.


```
.param pi = 4.0 * atan (1.0)
.param alpha = sqrt(2.0)


.param frequency = 20.0
.param w0 = 2.0 * pi * frequency

.model filter s_xfer (gain=1
+ num_coeff=[1.0 0.0 0.0]
+ den_coeff=[1.0 {w0*alpha} w0*w0]
+ int_ic=[0 0] denormalized_freq = 1.0)
```

```
a1 1 2 filter
```

and the response:

 

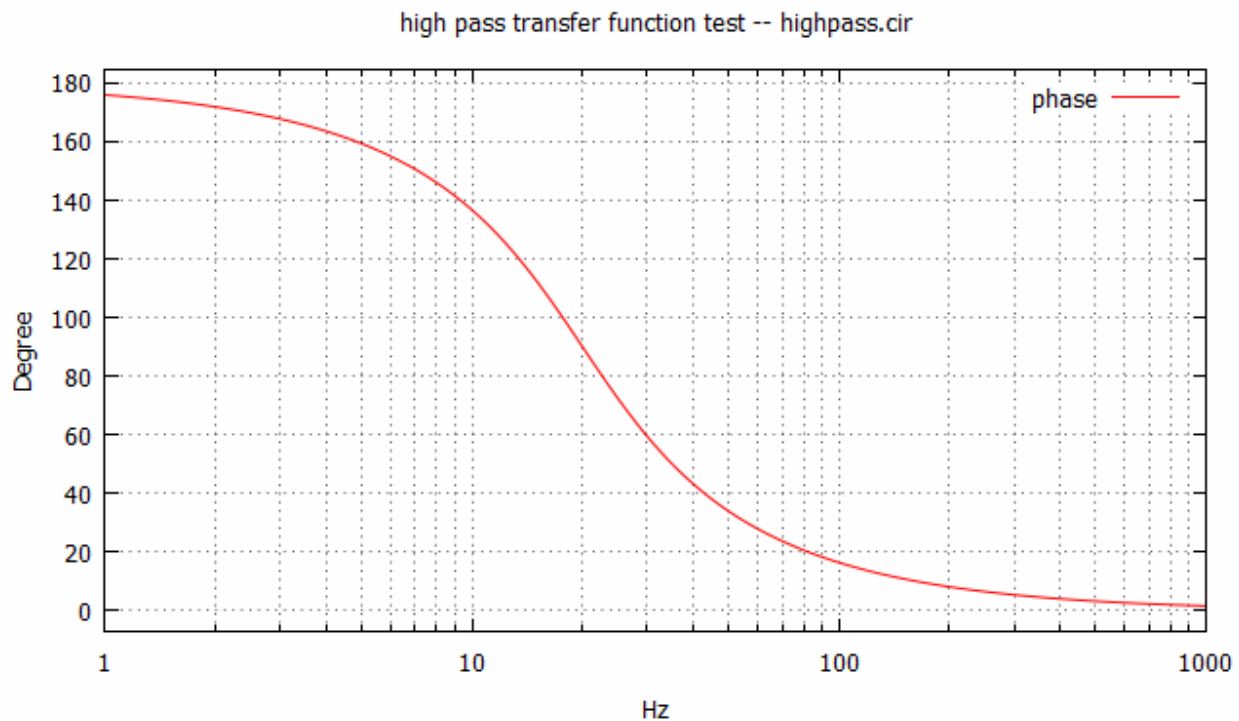

Scripting for the plots:

```
.control
destroy all

ac dec 1000 1 1000
let resp = db (v(2)/ v(1))
settype decibel resp

plot resp xlimit 6 100 ylimit -30 0
meas AC three_db_point WHEN resp=(-3.0)
meas AC six_db_point WHEN resp=(-6.0)
meas AC cutoff FIND resp AT=20.0

*
* Do the phase response.
*
let phase = 180.0/PI * cph (v(2) / v(1))
settype phase phase
plot phase title "High Pass Phase Response"
meas AC ninety_degrees WHEN phase = 90
.endc
```

The NGSPICE output:

ngspice 27 -> highpass.cir

Circuit: high pass transfer function test -- highpass.cir

Reducing trtol to 1 for xspice 'A' devices

Doing analysis at TEMP = 27.000000 and TNOM = 27.000000

Warning: v1: has no value, DC 0 assumed

```
No. of Data Rows : 3001
three_db_point      = 2.002380e+01
six_db_point        = 1.522080e+01
cutoff              = -3.010302e+00
ninety_degrees      = 2.000000e+01
```

Measurements

```
*
* Measure the period
*
meas TRAN period TRIG V(5) VAL=200m RISE=5 TARG V(5) VAL=200m RISE=6
let frequency = 1.0/period
print frequency
*
* Measure the duty cycle
*
meas TRAN period TRIG V(5) VAL=200m RISE=5 TARG V(5) VAL=200m RISE=6
meas TRAN pulse_width TRIG V(5) VAL=200m RISE=5 TARG V(5) VAL=200m FALL=5
let duty_cycle = 100.0* pulse_width/period
print duty_cycle
*
* Measure -3dB point, 0 dB max gain
*
meas AC three_db_point WHEN resp=(-3.0)
```

If the gain is greater than zero, the only way I have seen how to do this is to use these lines:

```
let measurement_point = vecmax (resp) - 3.0
meas AC lower_3dB WHEN resp = measurement_point RISE=1
meas AC upper_3dB WHEN resp = measurement_point FALL=1
```

Put FALL=1 if there is more than one falling edge. (I saw this once.)

```
*
* Measure rise time
*
meas TRAN range PP v(5)
let ten=0.1*range
let ninety=0.9*range
meas TRAN rise_time TRIG v(5) VAL=ten RISE=5 TARG v(5) VAL=ninety RISE=5
*
* Another rise/fall time measurement where PP voltage is trouble.
meas TRAN rise_time TRIG vout VAL=-100m RISE=3 TARG vout VAL= 100n RISE=3
meas TRAN fall_time TRIG vout VAL= 100m FALL=3 TARG vout VAL=-100n FALL=3
*
* Measure Q of a bandpass filter
*
    let pk = vecmax (resp)
    meas AC peak_frequency WHEN resp = pk
    meas AC lower_3dB WHEN resp = -3.0 RISE=1
    meas AC upper_3dB WHEN resp = -3.0 FALL=1
    let bw = upper_3dB-lower_3dB
    let q = peak_frequency/(upper_3dB-lower_3dB)
    print q
*
* Find the response at a specific frequency
*
meas AC cutoff FIND resp AT=20.0
```

```

*
* Find the time a peak occurs of a waveform after a transient simulation
*
meas TRAN peak_time MAX V(4)
*
* Find when the output is a given value as a function of X
*
meas DC temp_240 WHEN vout=240m
*
*Measure the time between two edges
*
meas TRAN tdiff TRIG vout1 RISE=3 VAL=1.0 TARG vout2 RISE=3 VAL=1.0
*
* Measure the RMS value of a waveform
*
meas TRAN rms_voltage RMS vout

```

FFT

```

Fourier Analysis Example --
four.cir

V1 1 0 SIN (0 1 440 0)
V2 2 0 SIN (0 1.7 1440 0 30)
V3 3 0 SIN (0 0.9 1234 0 55)

a2 [1 2 3] 4 sum1
.model sum1 summer
+ (in_gain=[1.0 1.0 1.0]
+ out_gain = 1.0)


.control
destroy all

tran 1e-6 200e-3
let sum = v(4)
gnuplot tran sum xlimit 0 30m

linearize sum
fft sum
let magnitude = mag(sum)
gnuplot mag magnitude xlimit 0
2k


.endc
.end

```

 


Pole-Zero Analysis and Transfer Function

Here is a simple circuit to analyze:

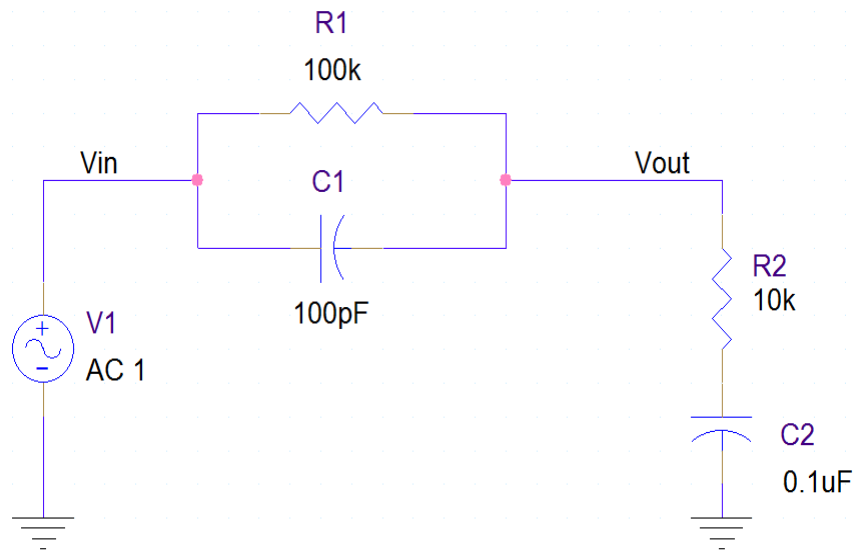

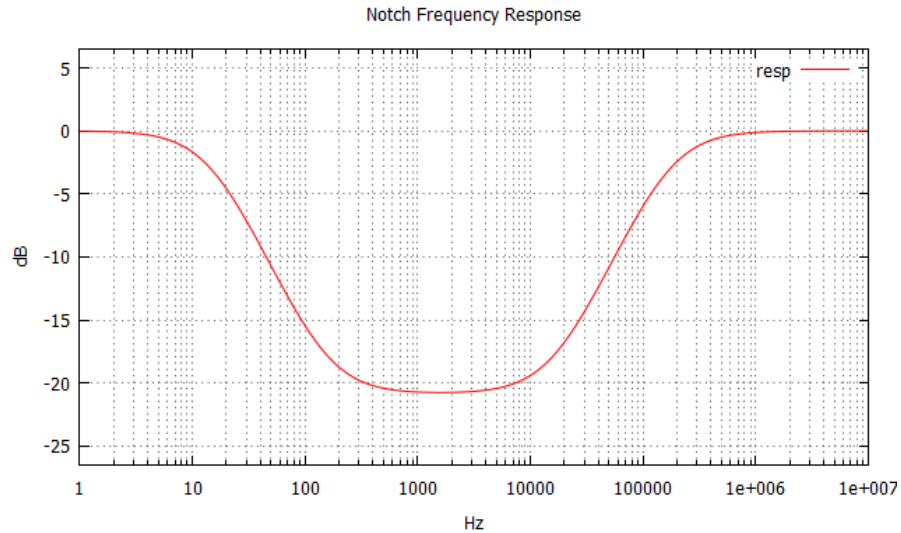This is lag-lead compensator from D'Azzo and Houpis, Linear Feedback and Control Systems, Synthesis and Design, McGraw Hill, New York.



The frequency response of this network is given below:

The pole-zero analysis yields:

```
pole(1) = -1.10091e+06,0.000000e+00
pole(2) = -9.08340e+01,0.000000e+00
zero(1) = -1.00000e+05,0.000000e+00
zero(2) = -1.00000e+03,0.000000e+00
```

And the transfer function report is:


```
transfer_function = 1.000000e+00
output_impedance_at_v(vout,0) = 1.000000e+05
v1#input_impedance = 1.000000e+20
```

And the commands for the control section to produce this output are:

```
pz Vin 0 Vout 0 vol pz
print all
tf v(vout, 0) v1          ; Notice v1 is a source, not a node!
print all
```

Fourier

See the switch circuit above.

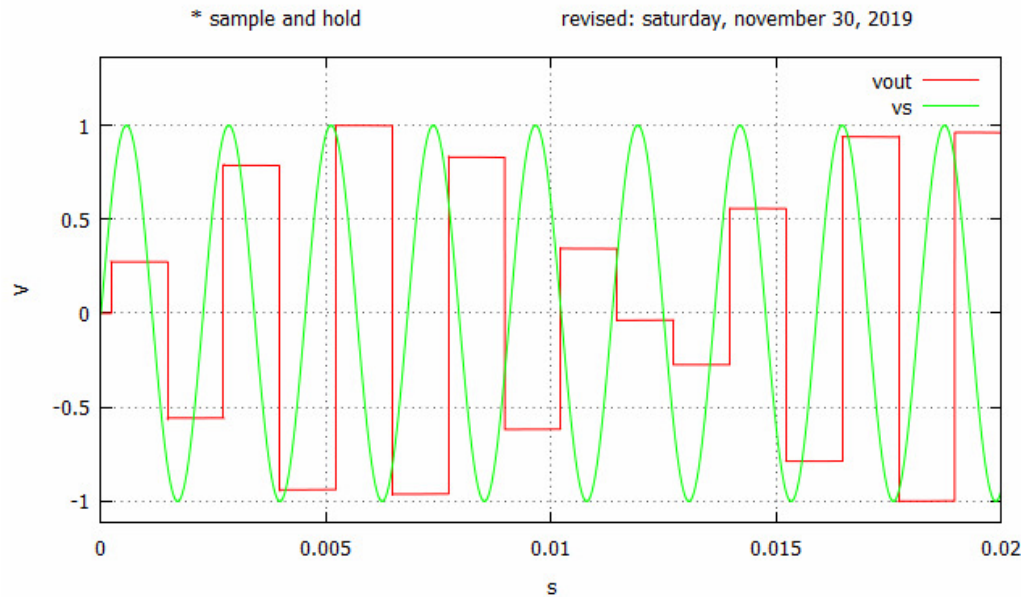

```
ngspice 66 -> fourier 440 vout
Fourier analysis for vout:
  No. Harmonics: 10, THD: 44.2091 %, Gridsize: 200, Interpolation Degree: 1
```

Harmonic	Frequency	Magnitude	Phase	Norm. Mag	Norm. Phase
0	0	-0.11667	0	0	0
1	440	1.23285	171.923	1	0
2	880	0.192827	-106.2	0.156408	-278.12
3	1320	0.370736	155.709	0.300716	-16.214
4	1760	0.18348	-122.4	0.148826	-294.32
5	2200	0.176647	139.508	0.143284	-32.415
6	2640	0.168498	-138.6	0.136674	-310.52
7	3080	0.0810902	123.311	0.0657748	-48.613
8	3520	0.148732	-154.8	0.120641	-326.72
9	3960	0.0217612	107.127	0.0176512	-64.796

Transient Simulation Trick

To alter the resistance during transient simulation, you may use a resistor like:

```
RS 1 0 R = 'TIME > 3m ? 2k : 1k'
```


Alter a sinusoidal source

```
alter @v1[sin] [ 0 $&newamp $&newfreq ]
```

[Alter Sinusoidal Source Reference](#)

Smith Chart

The following circuit is analyzed:

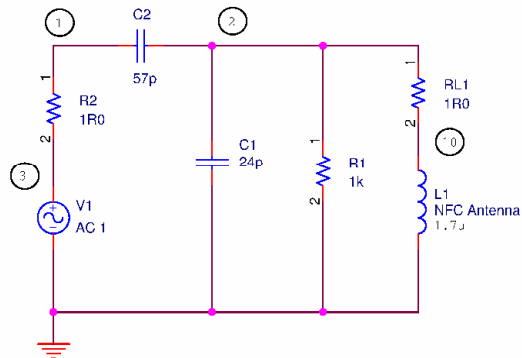

The netlist:

```
.TITLE  NFC Matching Network -- c.cir
R1  1 0 1000
L1  10 0 1.7u
RL1 10 1 1

C1 1 0 24p
C2 1 2 57p
R2 2 3 1


V1 3 0 sin (0, 1, 13.56E6) AC 1

.control
set color1 = black      ; set up the display colors
set color0 = white

ac dec 100 10E6 20E6
let z1=-v(3)/v1#branch  ; calculated the driving point impedance
settype impedance z1
plot z1

let zz=z1/50             ; normalize for the chart
settype impedance zz
plot zz smith

.endc
.end
```

 

The plot shows the impedance as seen by the input generator as a function of frequency. It can be seen at a frequency the impedance is 50 ohms, normalized on the chart.

Here are regions of the Smith Chart to give you a hint on how best to proceed:

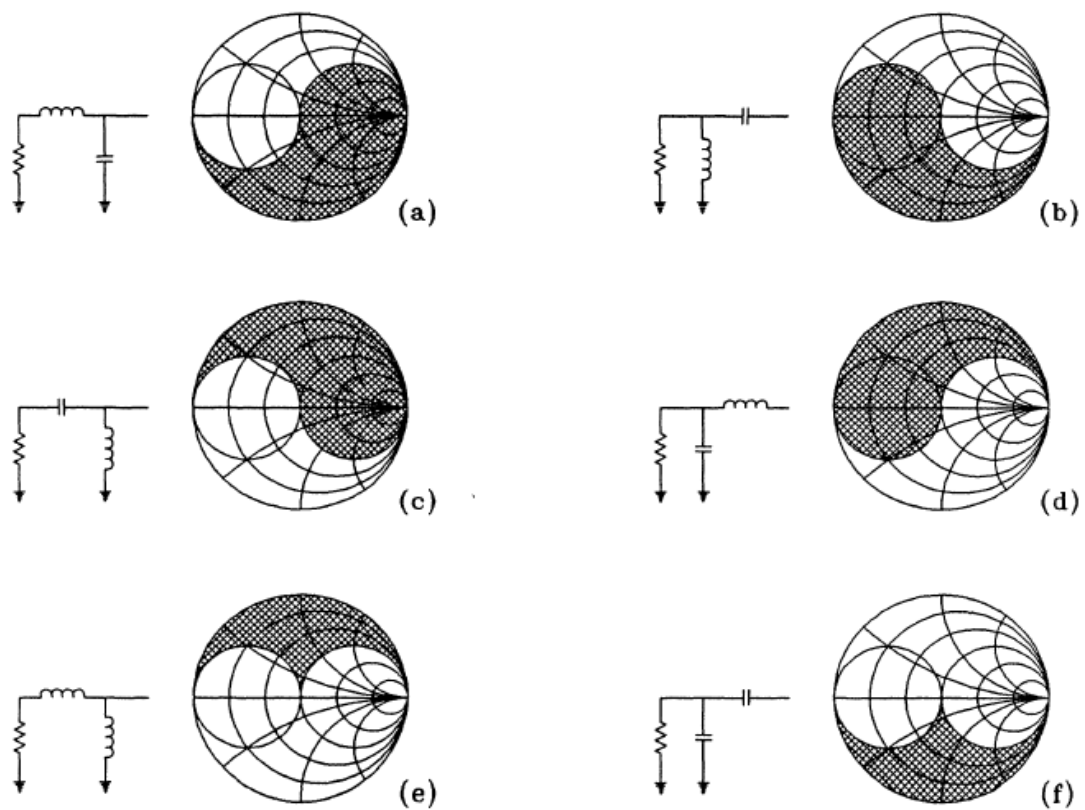


Figure 3.6 Matching regions for two-element networks.

From Medley, Microwave and RF Circuits: Analysis, Synthesis and Design, Artech House, Boston, London. Used with permission.

Gummel Plots

```
.TITLE NPN Gummel plot -- gummel.cir
*
* Creates Gummel data set from BJT model
*
.include "c:\SpiceModels\BJT\2N2369A.lib"
.include "c:\SpiceModels\BJT\bjt.lib"

V1 2 0 0
V2 3 0 12

Q1 3 2 0 2N3904

.control
set wr_singlescale

dc v1 0.35 1 0.01
let ic = -v2#branch
let ib = -v1#branch
let vbe = v(2)

wrdata gummel.txt vbe ic ib

.endc
.end
```


Data output sample:

```
6.90000000e-01 6.90000000e-01 2.86630295e-03 1.68741671e-05
7.00000000e-01 7.00000000e-01 4.14159168e-03 2.35835543e-05
7.10000000e-01 7.10000000e-01 5.94164201e-03 3.29793695e-05
7.20000000e-01 7.20000000e-01 8.44540163e-03 4.61284749e-05
7.30000000e-01 7.30000000e-01 1.18662520e-02 6.45018413e-05
7.40000000e-01 7.40000000e-01 1.64441373e-02 9.01048612e-05
7.50000000e-01 7.50000000e-01 2.24319010e-02 1.25627338e-04
7.60000000e-01 7.60000000e-01 3.00775557e-02 1.74594907e-04
7.70000000e-01 7.70000000e-01 3.96042577e-02 2.41483436e-04
```

Octave reading the table:

```
m=dlmread('gummel.txt');
```
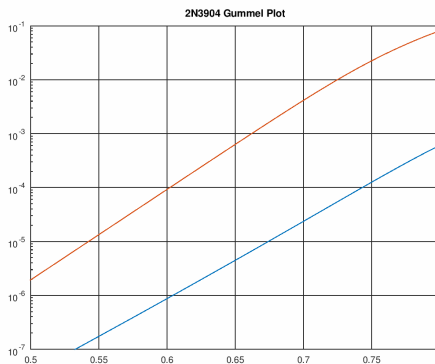
```
ic = m(:, 3);
ib = m(:, 4);
vbe = m(:, 2);
```





Results from various devices:

```
BC337 Maximum gain: 53.2 at Ic=0.00118846, Ib=2.58526e-006,
Vbe=0.600
2N2369A Maximum gain: 37.6 at Ic=0.859622, Ib=0.0112886,
Vbe=0.980
2N3904 Maximum gain: 45.3 at Ic=0.0118663, Ib=6.45018e-005,
Vbe=0.730
2N2222A Maximum gain: 46.2 at Ic=0.026325, Ib=0.000129467,
Vbe=0.730
2N5089 Maximum gain: 56.4 at Ic=0.00108467, Ib=1.64301e-006,
Vbe=0.620
MPSA18 Maximum gain: 63.3 at Ic=0.0258665, Ib=1.76724e-005,
Vbe=0.710
```

An Octave script processed the data and generated a common emitter netlist.

```
* ampx.cir Ic=0.0118663 Ib=6.45018e-005
Vbe=0.730
V12 12 0 9v
R1 12 2 10000
R2 2 0 3900
RC 12 5 470
Re 3 0 160
V3 5 4 0v
V1 0 1 SIN (0 0.001 1000) AC 1
Q1 4 2 3 2N3904 C1 1 2 0.00027

  C2 3 0 0.0047
C3 4 6 8.2e-005
RL 6 0 10k
.include "c:\SpiceModels\BJT\bjt.lib"
.control
tran 1e-7 5e-3
let vin = V(1)
let vout = V(6)
plot vin vout
ac dec 1000 2 200000
let resp = db (v(6) / v(1))
settype decibel resp
plot resp
.endc
.end
```



Parameterized Netlist for Device Selection

Netlist	Analysis
<pre>Parmaterized netlist trial -- p.cir * Device list: *----- * 1: 2n3904 * 2: 2n3906 * 3: MPS18 * .param device=3 ; device selector V1 2 0 0.7 V2 5 0 5 R1 5 1 10k .if (device = 1) Q1 1 2 0 2N3904 .elseif (device = 2) Q1 1 2 0 2N3906 .else Q1 1 2 0 MPSA18 .endif .include c:\SpiceModels\BJT\bjt.lib .control op print all .endc .end</pre>	<pre>ngspice 1 -> p.cir Circuit: parmaterized netlist trial -- p.cir Doing analysis at TEMP = 27.000000 and TNOM = 27.000000 No. of Data Rows : 1 v(1) = 6.329698e-03 v(2) = 7.000000e-01 v(5) = 5.000000e+00 v1#branch = -1.48829e-03 v2#branch = -4.99367e-04</pre>


Test Selector Mechanism

```
* This is the test selector.  Given tests may be turned on or off.
*
set transient = 1
set frequency_response = 1
set input_impedance = 0
set operating_point = 01
set reverse_voltage = 0
set power_dissipation = 1
set power_gain = 0
set capacitor_voltage = 0
set pulse_test = 1

if ($operating_point)
echo operating point
op
print all
end
```

Random voltage waveform
 
```
.TITLE Noise testing -- noisem1.cir  
VR1 1 0 dc 0 trrandom (2 1e-3 0 1) ; Gaussian  
V2 4 1 2.5  
  
.control  
tran 1e-6 200m  
plot v(1)  
.endc  
  
.end
```



The peak time is found measured as above:

```
meas TRAN peak_time MAX V(1)  
peak_time      = 2.260727e+000 at= 2.500000e-002
```

Using a File Source to Drive an Analog Design


This reads a digital waveform file and converts the digital signal via the bridge to analog. This is just a different way to generate an analog source rather than using the XSPICE filesource reading voltages.

```
.subckt filesource 1 2 3 4 5 6 7 8
A1 [11 12 13 14 15 16 17 18] input_vector
abridge1 [11 12 13 14 15 16 17 18] [1 2 3 4 5 6 7 8] dac1
.model input_vector d_source (input_file = "simple.txt")
.model dac1 dac_bridge(out_low = 0.12 out_high = 3.18 out_undef = 2.2
+ input_load = 5.0e-12 t_rise = 50e-9
+ t_fall = 20e-9)
.ends
```

Here is the input file:

```
*      a  b  c1 d  q  f  g  h
      0 0s 0s 0s 0s 0s 0s 0s 1s
100e-9 0s 0s 0s 0s 0s 0s 1s 0s
200e-9 0s 0s 0s 0s 0s 1s 0s 0s
300e-9 0s 0s 0s 0s 1s 0s 0s 0s
400e-9 0s 0s 0s 1s 0s 0s 0s 0s
500e-9 0s 0s 1s 0s 0s 0s 0s 0s
600e-9 0s 1s 0s 0s 0s 0s 0s 0s
700e-9 1s 0s 0s 0s 0s 0s 0s 0s
800e-9 0s 0s 0s 0s 0s 0s 0s 0s
900e-9 1s 1s 1s 1s 1s 1s 1s 1s
980e-9 0s 0s 0s 0s 0s 0s 0s 0s
```

Here are the generated waveforms:

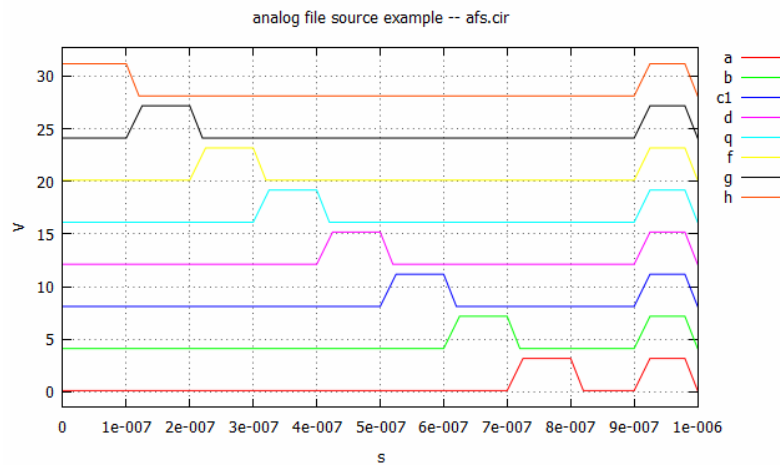

Vector Composition Example and a Reference Design

This demonstrates how to compare a reference design to your own design.

.TITLE Thorlabs Passive Filter Response vs Sallen-Key

```
V1 1 0 ac 1
V5 5 0 5
V6 6 0 -5
```

X1 1 10 5 6 filterlab3

```
.control
destroy all
```

```
*
* The reference design is here: https://www.thorlabs.com/thorproduct.cfm?partnumber=EF122#ad-image-0
*
```

```
* This is the reference design frequency response, in kHz
```

```
*
compose frequency_list values 4.00 5.42 7.36 8.91 10.79 13.18 14.76 16.24 18.03 19.84 20.01 20.19
21.27 22.02 23.41 24.66
+ 25.76 27.38 31.19 37.78 38.11 41.57 41.94 45.35 46.96 51.68 56.87 62.58 68.87 75.79 83.40 91.78
101.00 111.15 122.32 128.87
```

```
let frequency_list = frequency_list * 1000.0 ; scale the response to Hz
settype frequency_list ; correct the units
```

```
* This is a list of frequencies where the reference data was taken.
```

```
*
compose reference_list values (0.00) (-0.03) (-0.09) (-0.14) (-0.18) (-0.23) (-0.24) (-0.25) (-
0.26) (-0.28) (-0.28) (-0.29) (-0.37) (-0.50) (-0.99) (-1.91) (-3.12) (-6.25) (-14.87)
+ (-29.98) (-30.77) (-39.25) (-40.14) (-50.03) (-52.57) (-49.58) (-49.13) (-50.85) (-53.87) (-
58.15) (-66.20) (-69.13) (-64.11) (-60.65) (-58.90) (-58.29)
settype decibel reference_list ; correct the units.
```

```
* Analyze the design. Do this every 1 Hz to line up with the reference design data.
```

```
*
ac lin 150000 1 150000
let resp = db (v(10)/v(1))
settype decibel resp
```

```
* Create working vectors for the error computation and sampling the results of the analysis
```

```
*
let error = vector (length(frequency_list))
let sampled_resp = vector (length(frequency_list))
settype decibel sampled_resp
```

```
let index=0
```

```
*
* Loop through the reference design and compare the response at each
* frequency of the reference design to the Sallen-Key.
```

```
*
while index < length (frequency_list-1)
  let frequ = frequency_list[index] ; get a frequency from the list
  let result = resp [frequ] ; get a computed response at that frequency
  let sampled_resp[index] = result ; save it off

  let ref_value = reference_list[index] ; get the reference value

  let err = ref_value - result ; compute the error
  settype decibel err ; correct the units
  let error[index] = err ; save the error in the list
  let index = index + 1
end
```

```
settype decibel error
```

```
* Assign the vectors to more meaningful names for the plots.
```

```
*
let Sallen_Key = resp
let Thorlabs = reference_list
let computed_response = sampled_resp
*
```

```

* Plot the results
*
plot ylimit -55 2 xlog Sallen_key
plot ylimit -55 2 xlog Thorlabs computed_response vs frequency_list
plot xlog error vs frequency_list ylimit -10 5

```

```

.endc


```

```

.include filterlab3.lib          ; include the SPICE netlist from the Microchip Filterlab tool
.end

```

 This showed how the Sallen-key implementation compared to the purchased Thor Labs filter.



Some treasures are to be found here:

http://www.idea2ic.com/NGSPICE_TEMPLATES/NGSPICE%20TEMPLATES.html